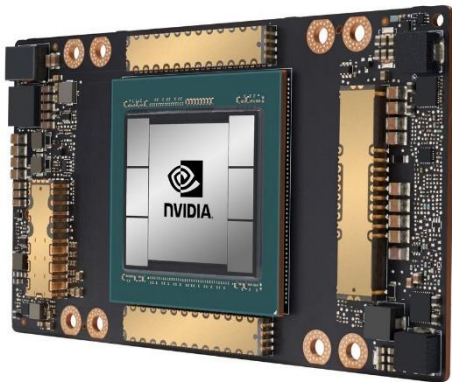



# CSCB58: Computer Organization



Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

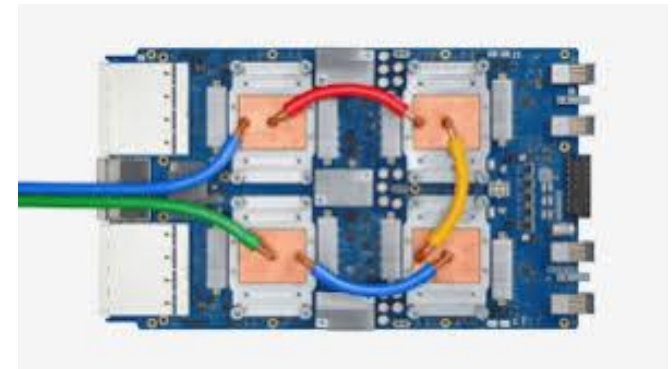

*The content of this lecture is adapted from the lectures of  
Larry Zheng and Steve Engels*

# **CSCB58 Week 4**

# Quiz 2 Discussion

# Question 2


Given the following Karnaugh Map, which one of the boolean expressions below represents the minimized logically equivalent formula?

$\downarrow VW \backslash$ $XY \rightarrow$	00	01	11	10
00	1	1	0	1
01	1	0	0	1
11	0	0	1	1
10	1	1	0	0


$$X'W' + V'Y' + XVW$$
 
# Question 5

Which of the following circuit diagrams represent a 2-to-1 multiplexer?  
Select all that apply



# New Topic: Sequential Circuits

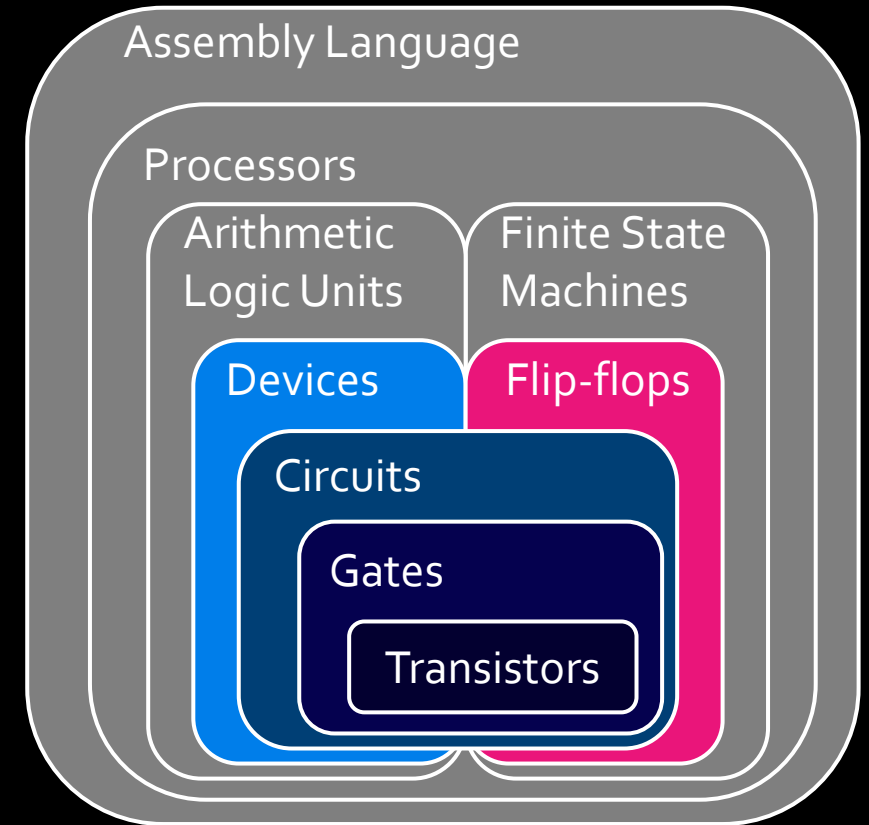

# Memory

Why do we have memory?

Why do circuits have memory?



# Something we can't do yet

- How does the Tickle Me Elmo work?

<https://www.youtube.com/watch?v=zG62dirxRgc>

- Same input, different outputs.
- The circuit somehow remembers how many pushes have been made.



# Two kinds of circuits

- So far, we've dealt with **combinational circuits**:
  - Circuits where the output values are entirely dependent and predictable from the input values.
- Another class of circuits: **sequential circuits**
  - Circuits that also depend on both the inputs and the **previous state** of the circuit.


# In other words...

- Combination circuits does NOT have memory
  - Everything is based on current input value
- Sequential Circuits have **memory**.
  - They **remember** something from the past (the previous state of the circuit), and its output depends on that
  - It is why computers have memory (e.g., RAM)


# Sequential circuits

- This creates circuits whose **internal state** can change over time, where the same input values can result in different outputs.
- Why would we need circuits like this?
  - Memory values
    - To remember stuff
  - Reacting to changing inputs
    - “Output  $X = 1$  when input A changes”

# How can a circuit have **memory**?

 

# Truth table of a sequential circuit

 


A	$Q_T$	$Q_{T+1} = A \cdot Q_T$
0	0	0
0	1	0
1	0	0
1	1	1

In these truth tables,  $Q_T$  and  $Q_{T+1}$  represent the values of Q at a time T, and a point in time immediately after (T+1)

The output not only depends on the input A, but also depends on the previous state of the circuit.

# AND with feedback

 


A	$Q_T$	$Q_{T+1} = A \cdot Q_T$
0	0	0
0	1	0
1	0	0
1	1	1

(0, 1, 0) is a transient state since it will become (0, 0, 0) immediately

Once the output is 0, it will be stuck at 0, no matter how you change A.

It has a memory that cannot be changed.


# NAND with feedback, more interesting

 

A	$Q_T$	$Q_{T+1}$	
0	0	1	Transient (-> (0, 1, 1))
0	1	1	
1	0	1	Oscillates between each other
1	1	0	


Output  $Q_{T+1}$  can be changed by changing A

# NAND waveform behaviour

 

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	1
1	0	1
1	1	0


Oscillates

 

Input A can control output Q, but the behavior of Q is not very stable.



# NOR with feedback

 

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	0
1	0	0
1	1	0

Oscillates between  
each other

Transient (-> (1, 0, 0))

Output  $Q_{T+1}$  can be changed by changing A

# Feedback behaviour

- NAND behaviour

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	1
1	0	1
1	1	0

- NOR behaviour

A	$Q_T$	$Q_{T+1}$
0	0	1
0	1	0
1	0	0
1	1	0



- What makes NAND and NOR feedback circuits different?
  - Unlike the AND and OR gate circuits (which get stuck), the output  $Q_{T+1}$  can be changed, based on A.
- However, gates like these that feed back on themselves could enter an unsteady state.

# Latch

A feedback circuit with (sort-of) stable behaviour

  
# Latches

- If multiple gates of these types are combined, you can get more steady behaviour.




- These circuits are called **latches**.

# S'R' Latch

 
 
# Warm up

This "locking" situation is typically a good starting point when analyzing the behaviour of a sequential circuit.





Knowing  $A = 0$ , what can you say about the output of the NAND gate?

- Must be 1, regardless of the other input
- i.e., a zero input **"locks"** the NAND gate

 
 
# S'R' latch: Case 1

- Let's see what happens when the input values are changed...
  - Assume that  $S'$  and  $R'$  are set to 1 and 0 to start.
  - The  $R'$  input sets the output  $Q'$  to 1, which sets the output  $Q$  to 0.
  - Setting  $R'$  to 1 keeps the output value  $Q'$  at 1, which maintains both output values.



 
 
# S'R' latch: Case 2

- (continuing from previous)
  - S' and R' start with values of 1, when S' is set to 0.
  - This sets output Q to 1, which sets the output Q' to 0.
  - Setting S' back to 1 keeps the output value Q at 0, which maintains both output values.







Whaaaaaf?!

 
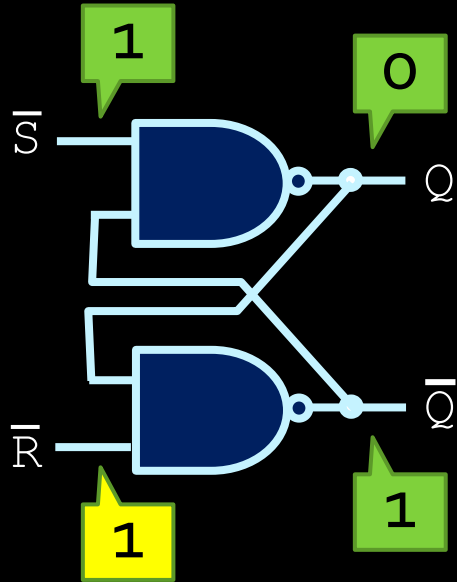


Same input, different outputs

  


Output of inputs 11 :

maintain the previous output!

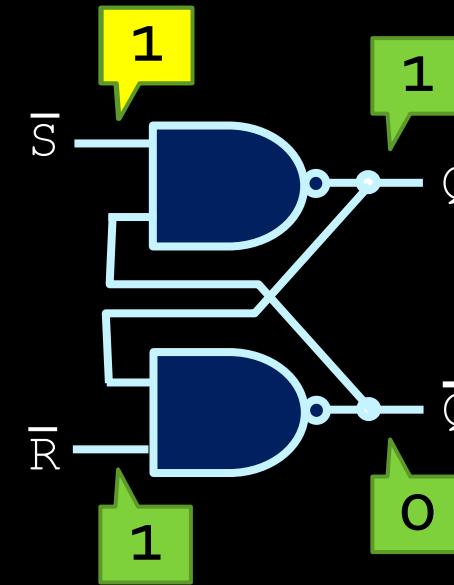 

# S'R' latch

 

$\bar{S}$	$\bar{R}$	$Q_T$	$\bar{Q}_T$	$Q_{T+1}$	$\bar{Q}_{T+1}$
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

- S and R are called “set” and “reset” respectively.
- When  $S' = 0$ ,  $R' = 1$ , Q is 1
- When  $S' = 1$ ,  $R' = 0$ , Q is 0
- When  $S'R' = 11$ , same as previous state (01 or 10)
- How about going from 00 to 11
  - Depends on whether it changes from 00 to 01 to 11, or from 00 to 10 to 11 (race condition)
  - **unstable behaviour**

# More on instability

- Unstable behaviour occurs when a  $S'R'$  latch goes from 00 to 11, or a SR latch goes from 11 to 00.
  - The signals don't change simultaneously, so the outcome depends on which signal changes first.
- Because of the unstable behaviour, 00 is considered a **forbidden state** in NAND-based  $S'R'$  latches, and 11 is considered a **forbidden state** in NOR-based SR latches.

# More on instability

$\bar{S}$	$\bar{R}$	$Q_T$	$\bar{Q}_T$	$Q_{T+1}$	$\bar{Q}_{T+1}$
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0

Forbidden state

$\bar{S}\bar{R}$ -latch


"set" and "reset"  
cannot be both true!

S	R	$Q_T$	$\bar{Q}_T$	$Q_{T+1}$	$\bar{Q}_{T+1}$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

SR-latch

Forbidden state


# SR latch, with NOR gates

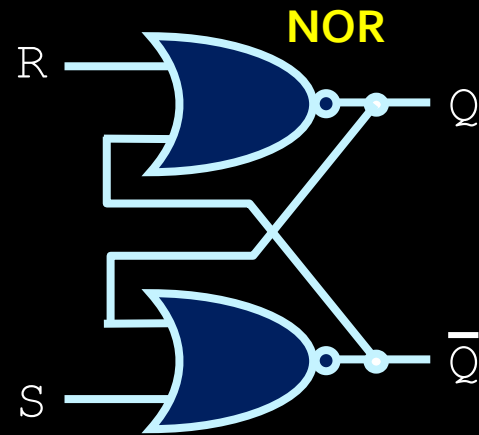

S	R	$Q_T$	$Q_T$	$Q_{T+1}$	$Q_{T+1}$
0	0	0	1	0	1
0	0	1	0	1	0
0	1	X	X	0	1
1	0	X	X	1	0
1	1	X	X	0	0

- In this case, S and R are simply "set" and "reset".
- In this case, the circuit "remembers" previous output when going from 10 or 01 to 00.
- As with  $\overline{S}\overline{R}$  latch, unstable behaviour is possible, but this time when inputs go from 11 to 00.

# Summary of S'R' / SR Latch behaviour

 

S: "set"; R: "reset"



$S = 1, R = 0: Q = 1$

$S = 0, R = 1: Q = 0$

$S = 0, R = 0: \text{"keep"}$
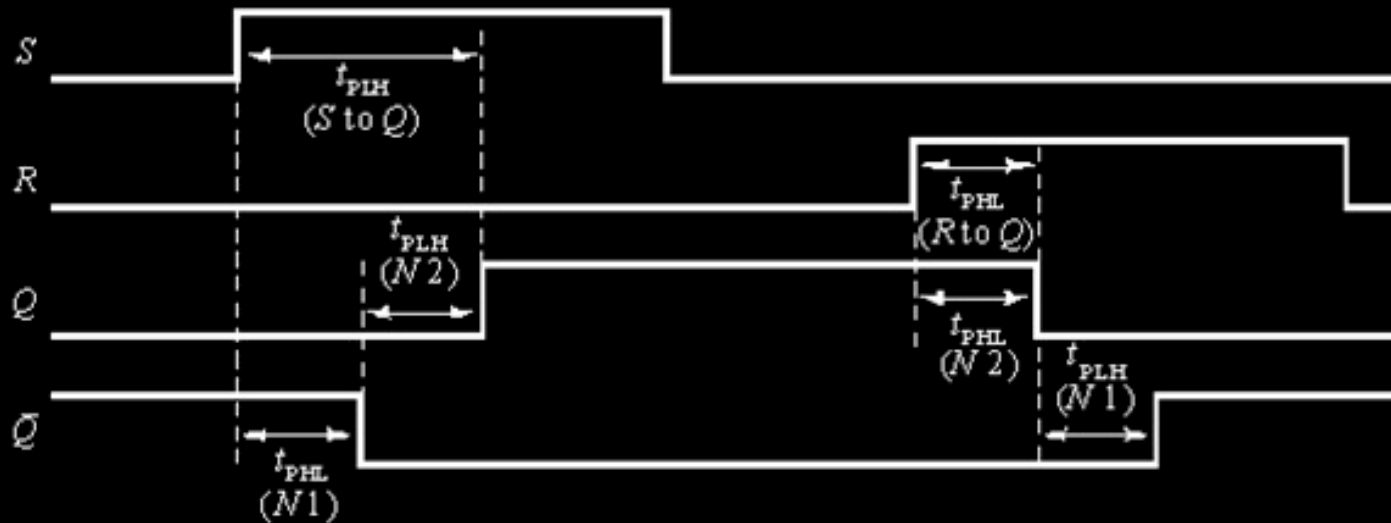 
# Be aware of delays

- Important to note that, in reality, the output signals don't change instantaneously, but with a certain delay.







# Reading from latches

- Now we have circuit units that can **store** high or low values.
- How do we distinguish
  - “5 highs in a row”
  - “10 highs in a row”
- We want to **sample** the signal with certain frequency.
- Need to use some sort of timing signal, to let the circuit know when the output may be sampled.

→ **clock signals.**
  
# Clock signals

- “Clocks” are a regular pulse signal, where the high value indicates that the output of the latch may be sampled.
- Usually drawn as:




- But looks more like (frequency is usually high):



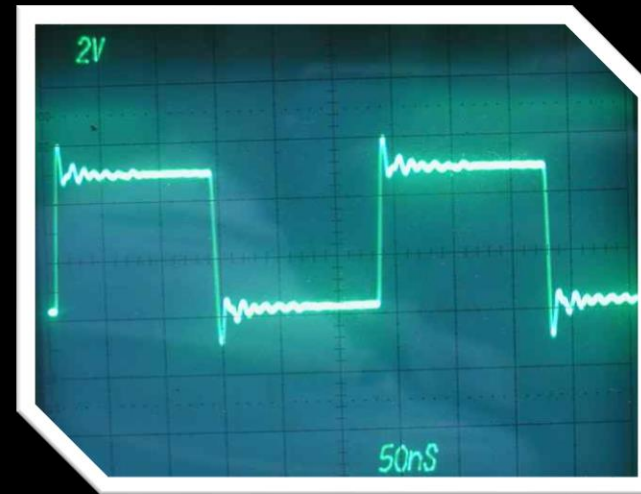
# Signal restrictions

- What's the limit to how fast the latch circuit can be sampled?
- Determined by:
  - latency time of transistors
    - Setup and hold time
  - setup time for clock signal
    - Jitter
    - Gibbs phenomenon
- **Frequency** = how many pulses occur per second, measured in Hertz (or Hz).
- What Intel and AMD try to increase every year.



# Clocked SR Latch


# Clocked SR latch

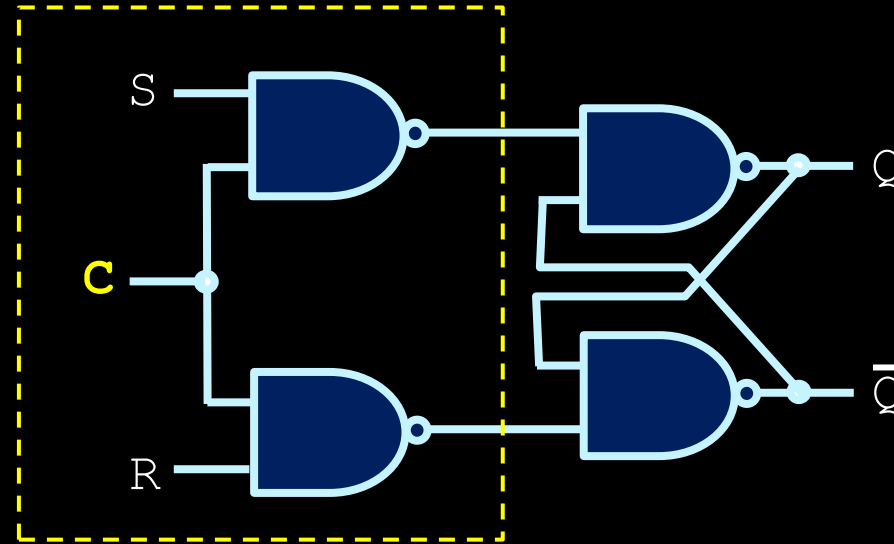

- By adding another layer of NAND gates to the  $\overline{S}\overline{R}$  latch, we end up with a **clocked SR latch** circuit.
- The clock is often connected to a pulse signal that alternates regularly between 0 and 1.

 
# Clocked SR latch behaviour


- Same behaviour as SR latch, but with timing:
  - Start off with  $S=0$  and  $R=1$ , like earlier example.
  - If **clock is high**, the first NAND gates invert those values, which get inverted again in the output.
  - Setting both inputs to 0 maintains the output values.


 
# Clocked SR latch behaviour

- Continued from previous:
  - Now set the **clock low**.
  - Even if the inputs change, the low clock input prevents the change from reaching the second stage of NAND gates.
  - Result: the clock needs to be high in order for the inputs to have any effect.



 


When clock is high, behave like a SR latch.

When clock is low, S and R are blocked and there is no way to change the output.




# Clocked SR latch

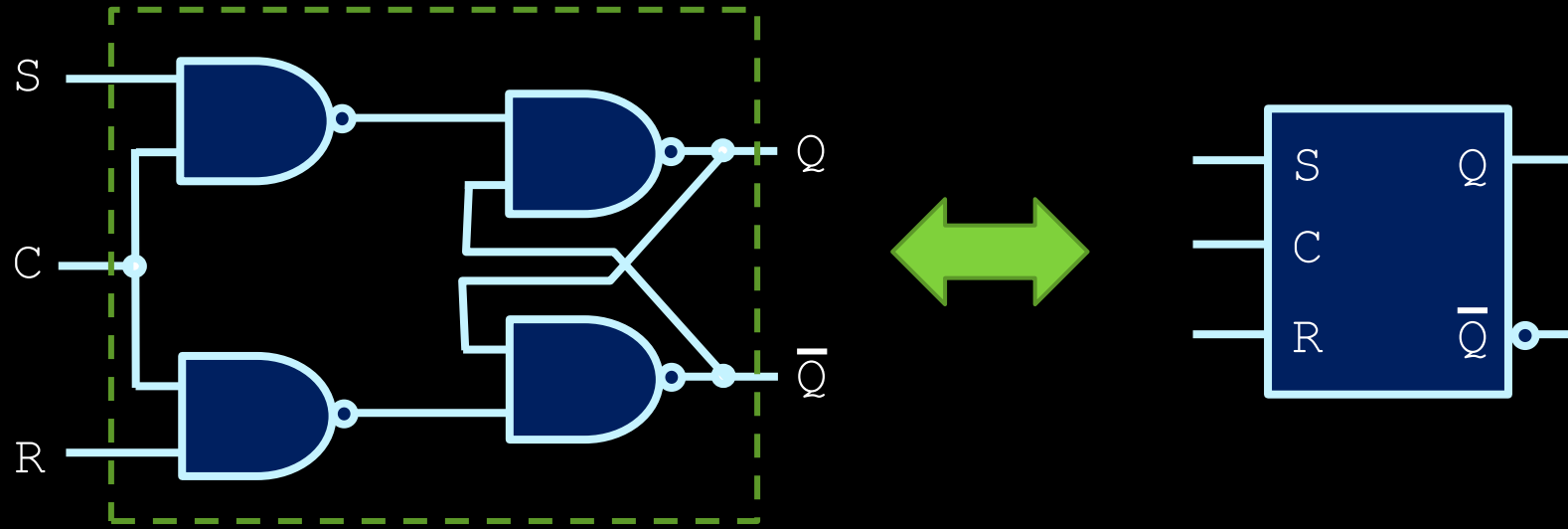

- This is the typical symbol for a clocked SR latch.
- This only allows the S and R signals to affect the circuit when the clock input (C) is high.
- Note: the small NOT circle after the  $\bar{Q}$  output is simply the notation to use to denote the inverted output value. It's not an extra NOT gate.

# Clocked SR latch behaviour

 


$Q_T$	S	R	$Q_{T+1}$	Result
0	0	0	0	no change
0	0	1	0	reset
0	1	0	1	set
0	1	1	?	???
1	0	0	1	no change
1	0	1	0	reset
1	1	0	1	set
1	1	1	?	???

- Assuming the clock is 1, we still have a problem when S and R are both 1, since it is the **forbidden state**.
  - Better design: prevent S and R from both going high.

# D latch

prevent S and R from both going high


# D latch

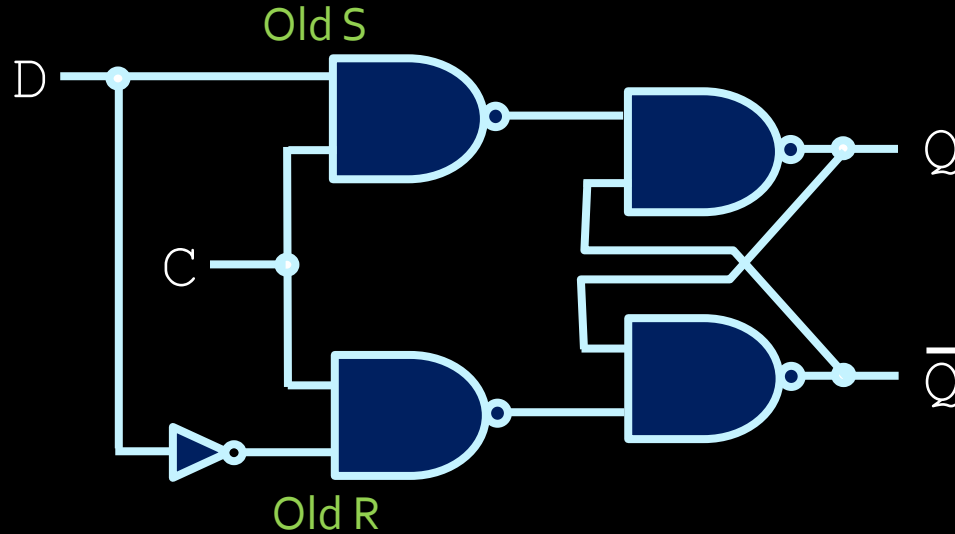

$Q_T$	D	$Q_{T+1}$
0	0	0
0	1	1
1	0	0
1	1	1

- By making the inputs to R and S dependent on a single signal D, you avoid the indeterminate state problem.
- The value of D now sets output Q low or high.


# D latch

 


- This design is good, but still has problems.
  - i.e. **timing issues**.
 
# Latch timing issues

- Consider the circuit on the right:
- When the clock signal is high, the output looks like the waveform below:





- Output keeps toggling back and forth.

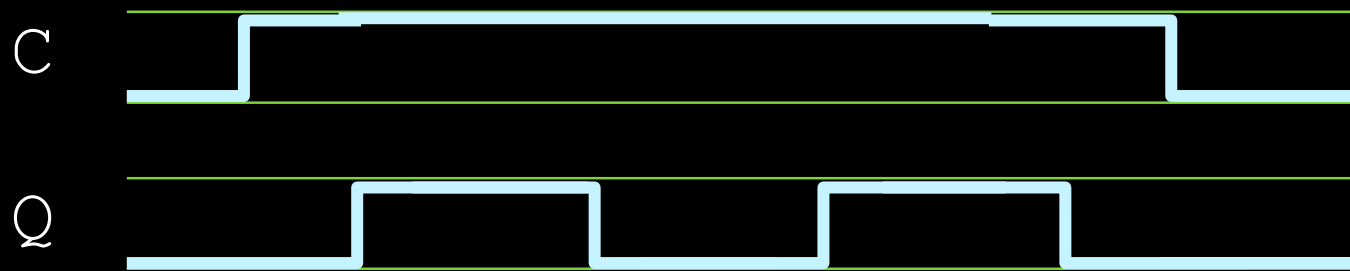

Would be nice if Q changes only **once** within **one clock cycle**


# Latch timing issues

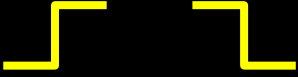 - Preferable behaviour:
  - Have output change only once when the clock pulse changes. 
  - Solution: create disconnect between circuit output and circuit input, to prevent unwanted feedback and changes to output.



Only one latch is active at one time, so in order for a change to propagate from input to output, you need to wait at least for one turn (a clock cycle) of both being active.


# Flip Flops

 




 
# SR master-slave flip-flop


- A **flip-flop** is a latched circuit whose output is triggered with the **rising edge** or **falling edge** of a clock pulse.
- Example: The SR master-slave flip-flop



 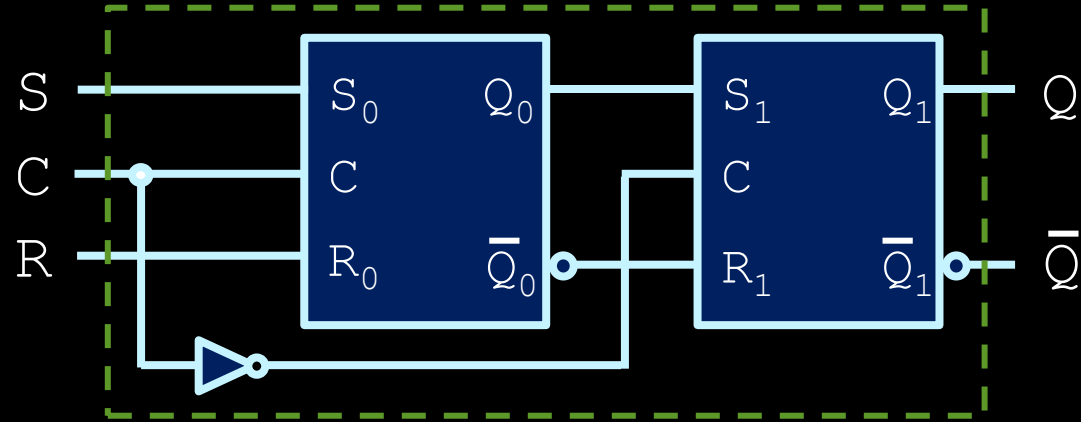
# Change of Q triggered by falling clock edges



# Edge-triggered D flip-flop


 


 - SR flip-flops still have issues of unstable behavior (**forbidden state**)
- Solution: **D flip-flop**
  - Connect D latch to the input of a SR latch.
  - **Negative-edge triggered** flip-flop (like the SR)



 
 
# Flip-flop behaviour

- Observe the behaviour:
  - If the clock signal is high, the input to the first flip-flop is sent out to the second.
  - The second flip-flop doesn't do anything until the clock signal goes down again.
  - When it clock goes from high to low, the first flip-flop stops transmitting a signal, and the second one starts.



  
# Flip-flop behaviour

- Continued from previous:
  - If the input to D changes, the change isn't transmitted to the second flip-flop until the clock goes high again.
  - Once the clock goes high, the first flip-flop starts transmitting at the same time as the second flip-flop stops.


 
# Edge-triggered flip-flop


- Alternative: **positive-edge triggered** flip-flops




- These are the most commonly-used flip-flop circuits (and our choice for the course).

# Notation

- Latches


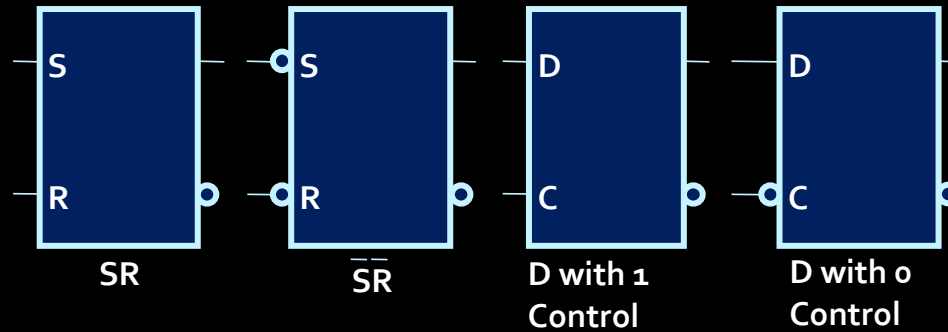


- Edge-triggered flip-flops

 
  
# Other Flip-Flops

- The **T flip-flop**:
  - Like the D flip-flop, except that it toggles its value whenever the input to T is high.







# Other Flip-Flops

- The **JK Flip-Flop**:


- Takes advantage of all combinations of two inputs (J & K) to produce four different behaviours:

  - if J and K are 0, maintain output.
- if J is 0 and K is 1, set output to 0.
- if J is 1 and K is 0, set output to 1.
- if J and K are 1, toggle output value.


 
# Sequential circuit design

- Similar to creating combinational circuits, with extra considerations:
  - The flip-flops now provide extra inputs to the circuit
  - Extra circuitry needs to be designed for the flip-flop inputs.
  - ...which is next week's lecture 😊




## Today we learned

- Sequential circuits – circuits with memory
- Latch
- Flip-flop

## Next week

- Registers, Counters
- Finite State Machines
- Sequential circuit design


# CSCB58: Computer Organization

 

Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

 

*The content of this lecture is adapted from the lectures of  
Larry Zheng and Steve Engels*